



COMSATS University Islamabad, Lahore Campus

Department of Computer Engineering

Quiz # 3

Course Title:	VLSI Design	Course Code:	CPE434	Credit Hours:	4(3,1)
Course Instructor:	Dr. Muhammad Naeem Awais	Programme Name:	BS Computer Engineering		
Semester:		Batch:		Date:	11 st May 2026
Time Allowed:	10 Minutes		Maximum Marks:	5	
Student's Name			Registration. No.:		

Question # 1:

(PLO3-CLO3-C5)

Design a circuit for the following function at transistor level with LEAn integration with Pass transistors:

$$F(A,B,C) = \sum(0,2,4,5,7)$$

$$F(A,B,C) = \sum(0,2,4,5,7)$$

$$= A'B'C' + A'BC' + AB'C' + ABC' + ABC$$

$$= A'(1 \cdot B' \cdot C' + 1 \cdot B \cdot C' + 0 \cdot B' \cdot C' + 0 \cdot B' \cdot C + 0 \cdot B \cdot C) \\ + A(0 \cdot B' \cdot C' + 0 \cdot B \cdot C' + 1 \cdot B' \cdot C' + 1 \cdot B' \cdot C + 1 \cdot B \cdot C)$$

$$= A'(B'C' + BC') + A(B'C' + B'C + BC)$$

$$B'C' + BC' = B'(1 \cdot C' + 0 \cdot C') + B(0 \cdot C' + 1 \cdot C') \\ = B'(C' + 0) + B(0 + C') = B'(C') + B(C')$$

$$\begin{aligned}
 B'C' + B'C + BC &= B'(1 \cdot c' + 1 \cdot c + 0 \cdot c) + B(0 \cdot c' + 0 \cdot c + 1 \cdot c) \\
 &= B'(c' + c + 0) + B(0 + 0 + c) \\
 &= B'(c' + c) + B(0 + c) \\
 &= B'(1) + B(c)
 \end{aligned}$$

