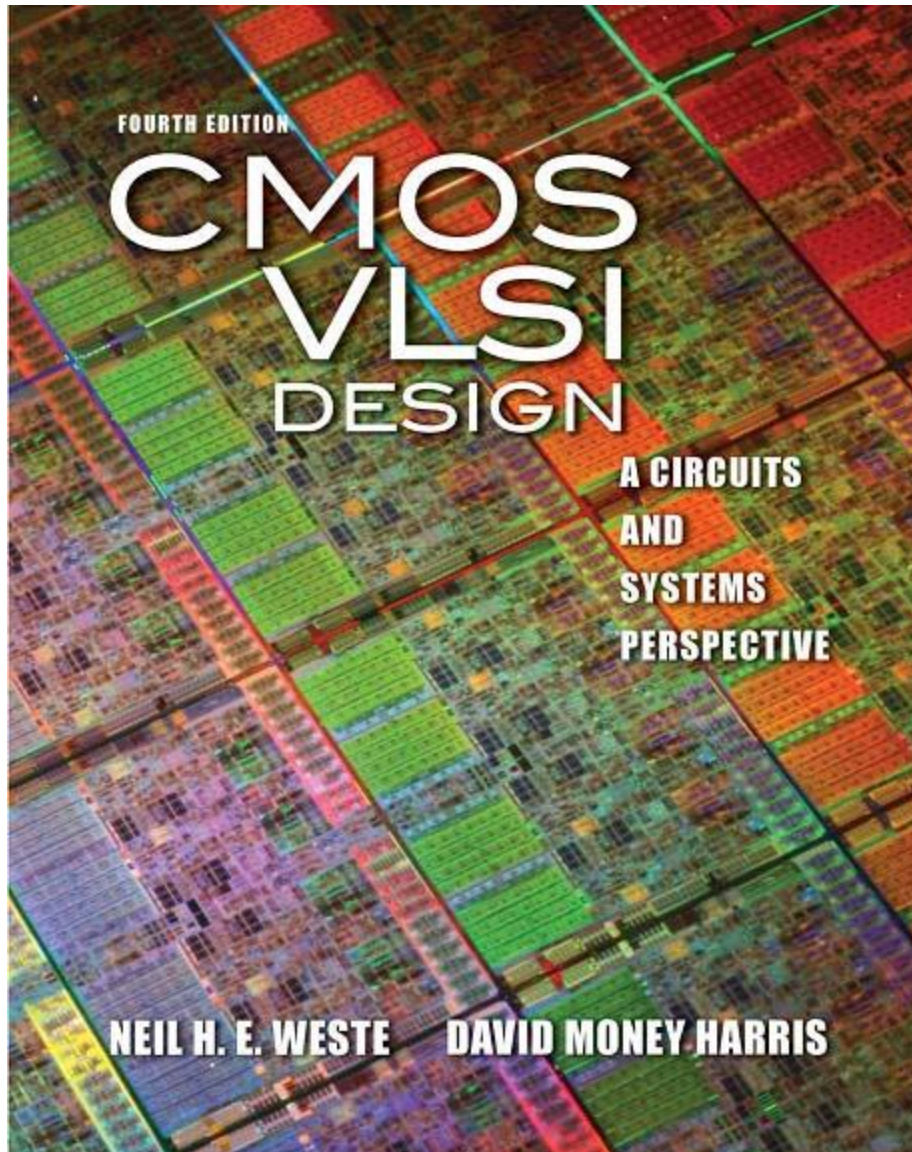




Array Subsystems

Lecture # 4

- ❑ Boolean Function Implementation with ROM
- ❑ Programmable Logic Arrays
 - PLA
 - PAL
 - Boolean Function Implementation with PLA
 - Boolean Function Implementation with PAL

Boolean Function Implementation with ROM





❑ $F_0 = A$

❑ $F_1 = A'B' + AB$

A	B	F_0	F_1
0	0	0	1
0	1	0	0
1	0	1	0
1	1	1	1

❑ $F_0 = AB' + AB$

❑ $F_1 = A'B' + AB$

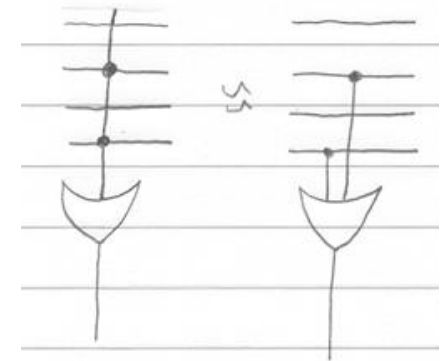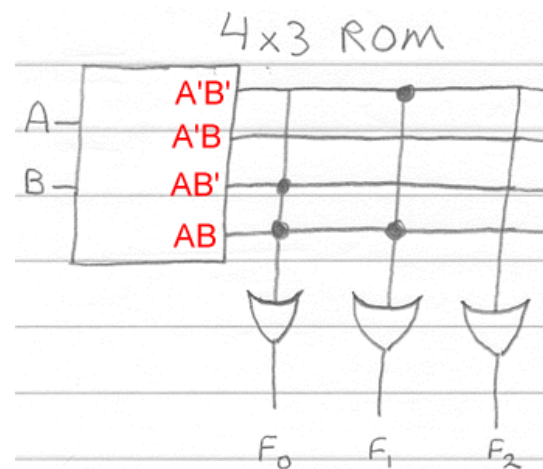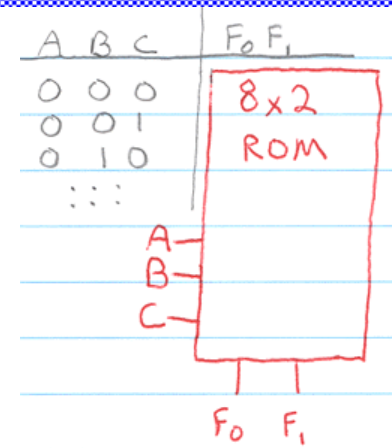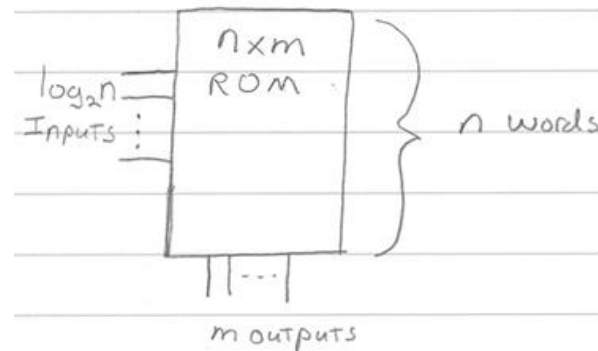


PLAs

- ❑ A *Programmable Logic Array* performs any function in sum-of-products form.
- ❑ *Literals*: inputs & complements
- ❑ *Products / Minterms*: AND of literals
- ❑ *Outputs*: OR of Minterms

- ❑ Example: Full Adder



$$s = a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}c + abc$$

$$c_{\text{out}} = ab + bc + ac$$

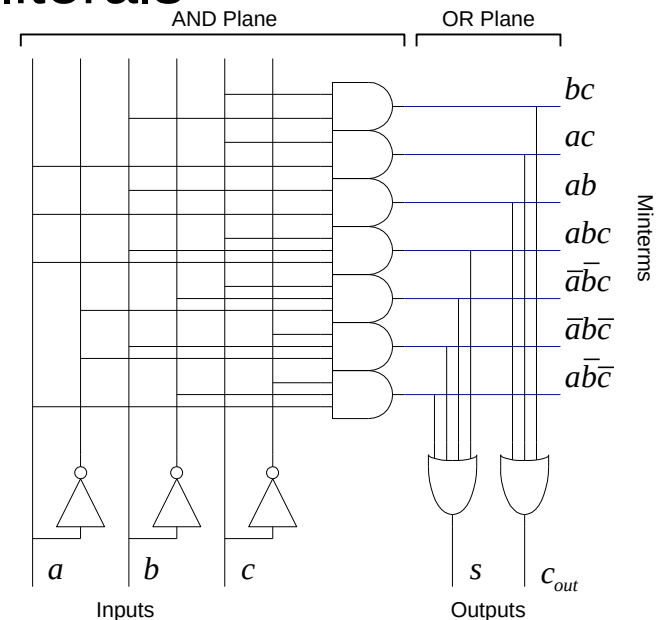


NOR-NOR PLAs

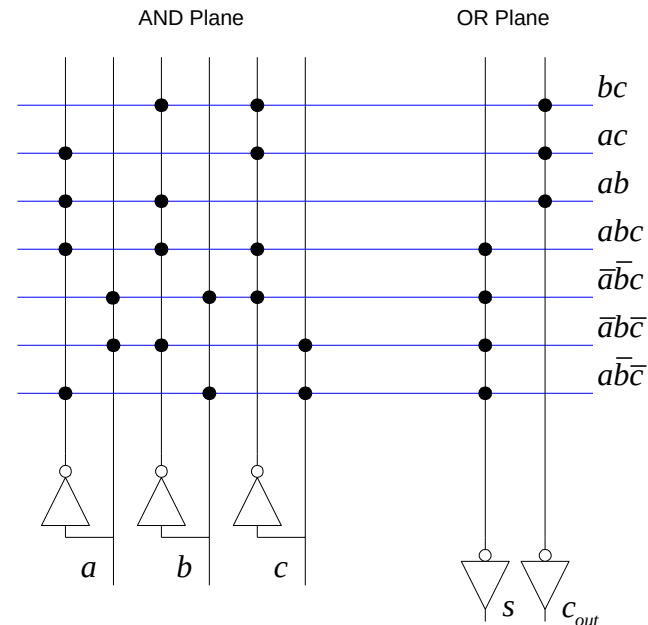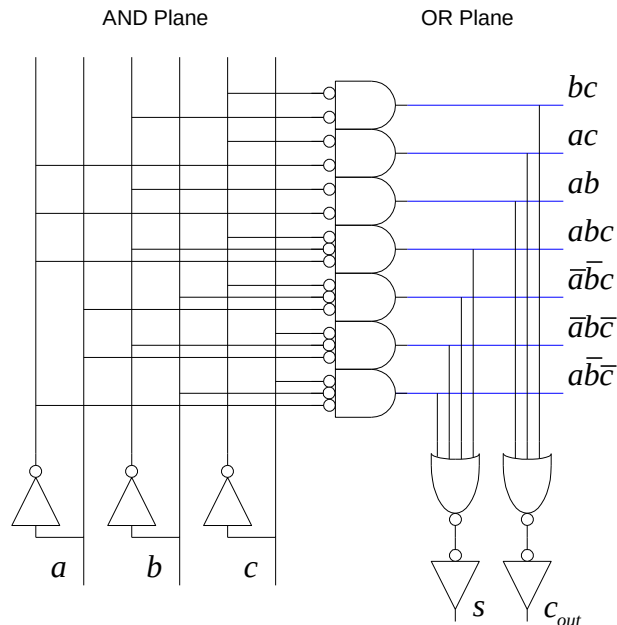- ❑ ANDs and ORs are not very efficient in CMOS
- ❑ Dynamic or Pseudo-nMOS NORs are very efficient
- ❑ Use DeMorgan's Law to convert to all NORs



PLA Schematic


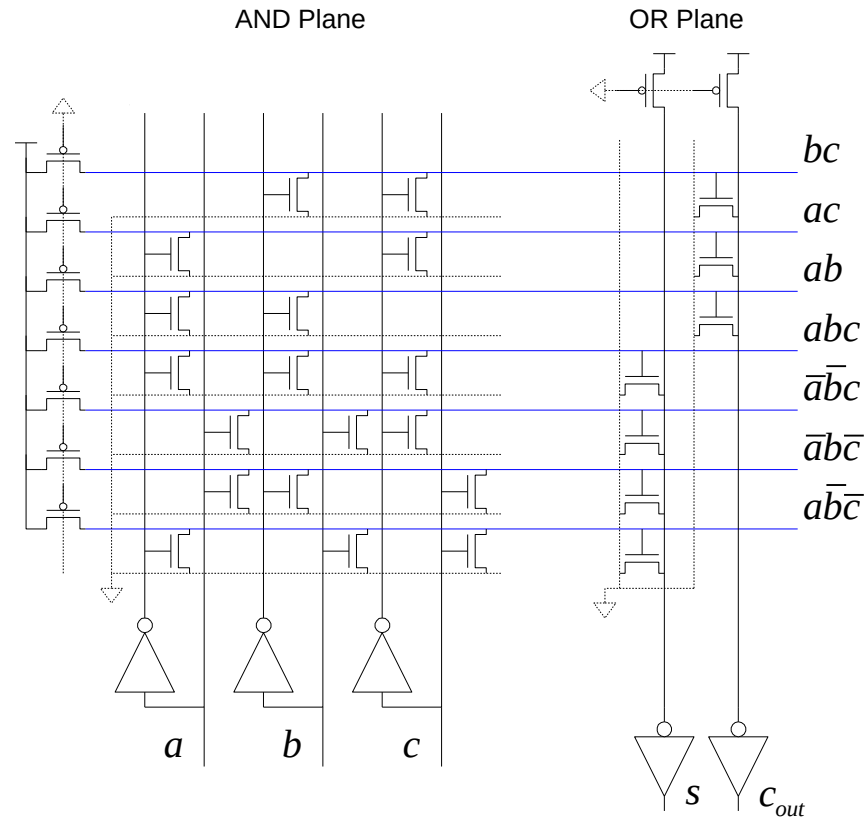


PLAs vs. ROMs

- ❑ The OR plane of the PLA is like the ROM array
- ❑ The AND plane of the PLA is like the ROM decoder
- ❑ PLAs are more flexible than ROMs
 - No need to have 2^n rows for n inputs
 - Only generate the minterms that are needed
 - Take advantage of logic simplification



Boolean Function Implementation with PLA

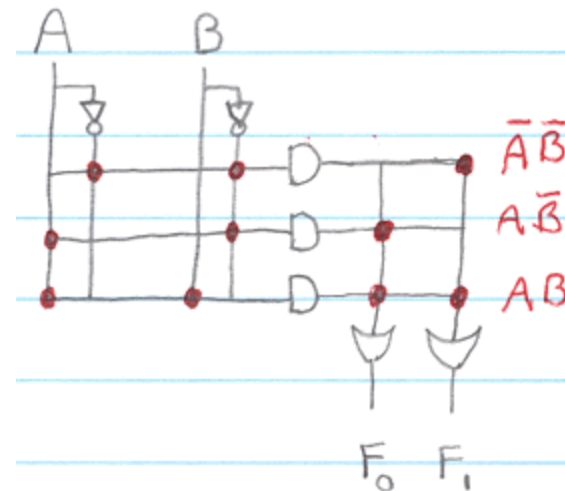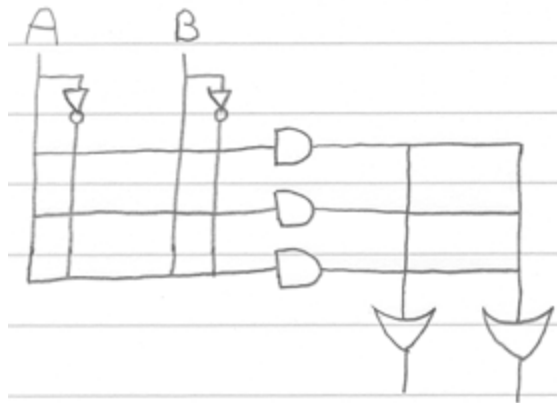- ❑ A PLA is a programmable logic device with a programmable AND array and a programmable OR array.
- ❑ $F_0 = A$
- ❑ $F_1 = A'B' + AB$



Boolean Function Implementation with PAL

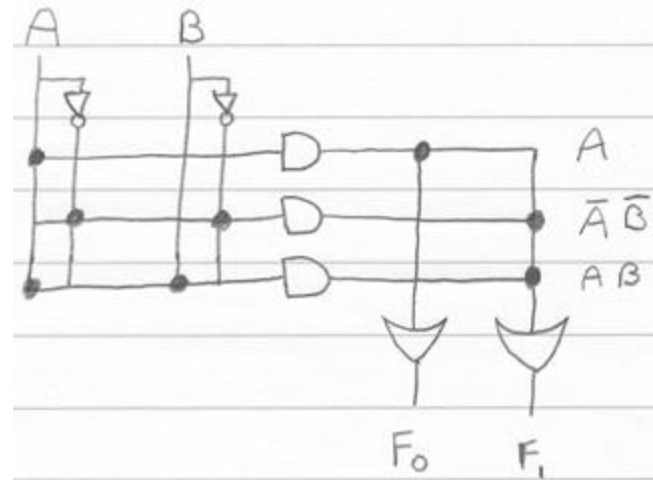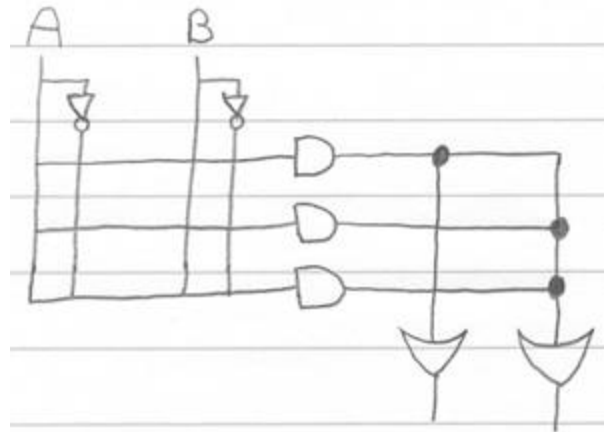- ❑ A PAL is a programmable logic device with a programmable AND array and a fixed OR array.
- ❑ $F_0 = A$
- ❑ $F_1 = A'B' + AB$



Comparison

- ❑ A PLA device has a programmable AND and programmable OR array
- ❑ A PAL device has a programmable AND and fixed OR array
- ❑ (You could also say that a ROM has a fixed AND and programmable OR array)

Home Work

- ❑ Implement the Sum output of Full Adder through ROM, PLA and PAL at transistor level.